

Name:

Date:

Class:

In a Row Math Worksheet



1. Draw a circuit diagram for a circuit that has one battery and two light bulbs connected in series.

2. For the above circuit, one bulb has a resistance of $2\ \Omega$ and a second bulb has a resistance of $3\ \Omega$. The total resistance for two bulbs in series is equal to the sum of their resistances.

Use this equation to find the total resistance of the circuit: $R_{\text{total}} = R_1 + R_2$

3. For a circuit that has one battery and two light bulbs connected in series, one bulb has a resistance of $1\ \Omega$, and the total resistance of the circuit is $6\ \Omega$. What is the resistance of the second light bulb?

4. If a circuit has two $1.5\ \text{V}$ batteries in series, what is the voltage across the two batteries?

5. If a circuit has two $1.5\ \text{V}$ batteries in series and one $3\ \Omega$ light bulb, what is the current in the circuit?

Use the Ohm's law equation: $I = \frac{V}{R}$