

Name:

Date:

Class:

Make a Battery Worksheet

1. Draw a picture of the potato battery setup in the space below. Label the **potato**, **wire**, and **light bulb** parts. Draw **arrows** to show the direction of the current.

2. How does the potato help the circuit to work?

3. Why must engineers understand circuits when making electrical appliances?
